

Subject: Analog system and application

Class: Bsc (Hon) Phy.

Assignment #

Define

1. Inverting and Non Inverting Amplifier

2. Define Adder op-Amp.

3. Define Subtractor op-Amp.

4. Define Integrator op-Amp.

5. Define Log amplifier